

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -1 EXAMINATION- 2023

B.Tech-III Semester (ECE)

COURSE CODE (CREDITS): 18B11EC313 (4)

MAX. MARKS: 15

COURSE NAME: ELECTRONIC DEVICES AND CIRCUITS

COURSE INSTRUCTORS: Dr. Shruti Jain

MAX. TIME: 1 Hour

Note: (a) All questions are compulsory.

(b) Marks are indicated against each question in square brackets.

(c) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems

Section A (Short Answers : $1 \times 5 = 5$ marks) [CO1]

1.

- i. If in a metal, the charge, mobility and concentration of electron are represented by q , μ , and n respectively, the electrical conductivity of the metal is _____
- ii. Nisha wants to study about mass action law and Einstein relationship. Help her in explaining the two considering n- type semiconductor.
- iii. Total hole current is a sum of _____ and _____ current.
- iv. The p -side of a diode is connected to ground and the n -side is given a potential of 2V. Then the diode will be in _____. The depletion layer of PN junction is increased when the junction is _____ bias.
- v. The _____ circuit clips off the entire positive half cycle of the input applied voltage. The _____ circuit is a circuit in which the output voltage can be shifted at a specific voltage level.

Section B (Long Answers : $2 \times 5 = 10$ marks) [CO1]

2. Find the conductivity of a Germanium semiconductor at 300K if donor impurity is $N_D = 4.5 \times 10^{27}/\text{m}^3$. Determine the minority carrier density. Assume $n_i = 2.5 \times 10^{19}/\text{m}^3$, $\mu_n = 0.23 \text{ m}^2/\text{V-s}$, and $\mu_p = 0.05 \text{ m}^2/\text{V-s}$.
3. At room temperature of 300K, the fermi level is 0.25eV below the conduction band in an N-type semiconductor. When the temperature is increased to 400K, calculate the position of the Fermi level.

- Justify the statement "PN junction diode is nonlinear device".
- A Zener diode shunt regulated power supply is depicted in Fig 1 . Determine (a) Output voltage, (b) source current, and (c) current through the Zener diode. Assume zener resistance is equal to zero.

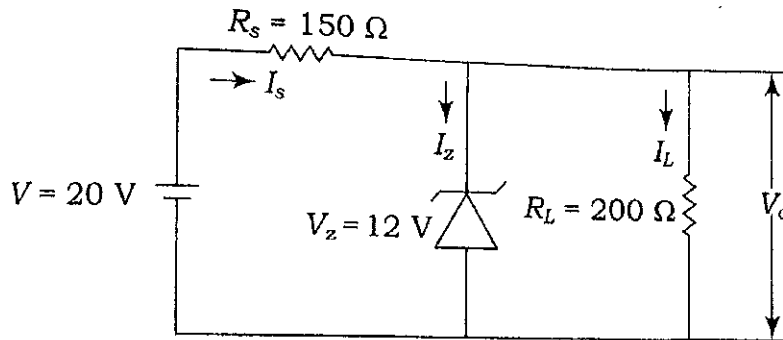


Fig 1

- Shyam wants to evaluate the efficiency of the single-phase full wave rectifier circuit using centre tapped transformer as shown in Fig 2. Help him in doing so. Assume $R_f = 0$.

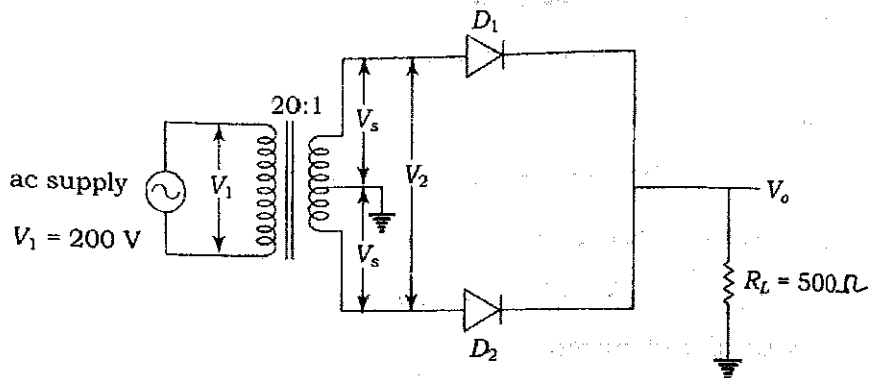


Fig 2