

Do soufi

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT
 MID TERM (SUMMER SEMESTER EXAMINATION)- June-2018

B.Tech.

COURSE CODE: 10B11EC111

MAX. MARKS: 50

COURSE NAME: ELECTRICAL CIRCUIT ANALYSIS

COURSE CREDITS: 04

MAX. TIME: 2 Hrs

Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.

1. Find the current through 4-Ω resistor in the circuit shown in Fig. 1, using superposition theorem.

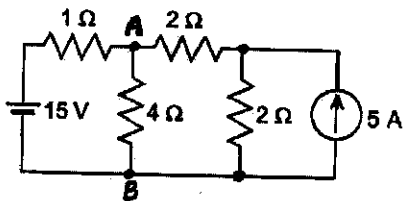


Fig 1

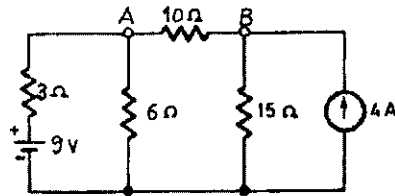


Fig 2

2. Find the current I in 10-Ω resistor in the circuit shown in Fig 2, using Thevenin's theorem.
 3. In the circuit shown in Fig. 3, find the current I_R by using Norton's theorem.

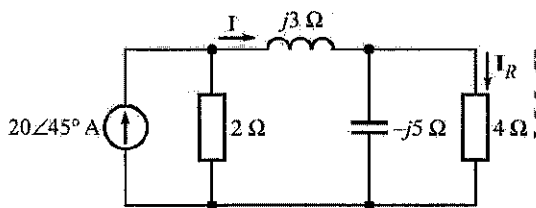


Fig 3

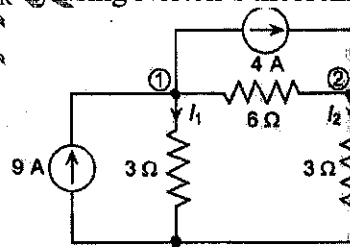


Fig 4

4. a) By applying nodal analysis to the circuit in Fig. 4, determine the currents I_1 and I_2 .
 b) Use KCL, KVL and Ohm's law to find v_2 , v_3 , i , R_1 and R_3 , in the circuit of Fig. 5.

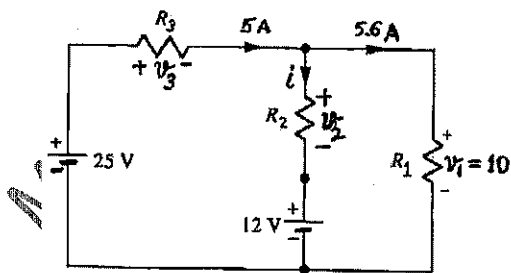


Fig 5

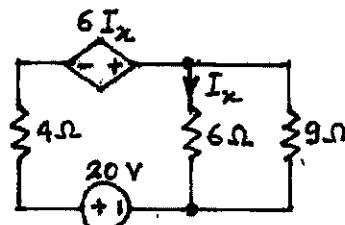


Fig 6

5. Find the current in the 9-Ω resistor of the circuit shown in Fig. 6, using Thevenin's theorem.