

JAYPEE UNIVERSITY OF INFORMATRION TECHNOLOGY, WAKNAGHAT

SUMMER SEMESTER EXAMINATIONS-T1- July, 2018

B. Tech (ECE), III Semester

COURSE CODE: 10B11EC312

MAX. MARKS: 50

COURSE NAME: Analog Electronics

COURSE CREDITS: 04

MAX. TIME: 2 HRs

Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.

Q.1. Define the following terms:

10

- (i) Mass action law
- (ii) PN Junction
- (iii) Fermi level
- (iv) Einstein relation ship
- (v) Mean life time charge carriers
- (vi) Recombination
- (vii) Drift Current
- (viii) Diffusion current
- (ix) Diode Capacitances
- (x) Varactor diode

Q.2 (i) Compare the BJT and JFET

04

(ii) Draw the input and output characteristics of BJT for CB, CE configurations


04

(iii) Establish the relation between α , β , and γ where these are associated with BJT configurations.

04

Q.3. (i) Find the z_0 for the following circuit:

02

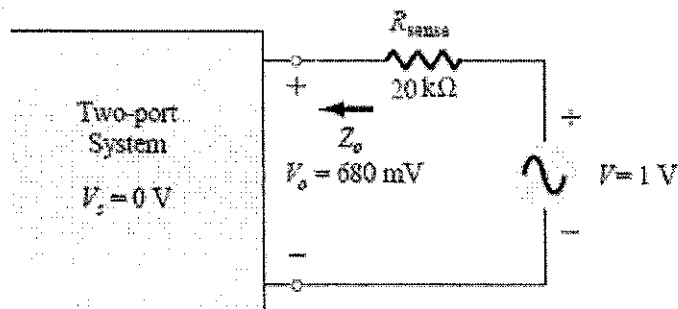(ii) Find the following parameters if $\beta = 120$, $I_E = 3.2\text{ mA}$, $r_o = \infty$ for CE configuration.

04

- (a) Z_i (b) A_V if load $2\text{ k}\Omega$ is applied (c) A_i if load $2\text{ k}\Omega$