

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT
TEST -2 EXAMINATION- 2024

B.Tech-II Semester (BI/BT)

COURSE CODE(CREDITS): 18B11EC212(4)

MAX. MARKS: 25

COURSE NAME: Basic Electrical Science

COURSE INSTRUCTORS: Dr. Alok Kumar

MAX. TIME: 1 Hour 30 Minutes

Note: (a) All questions are compulsory.

(b) Marks are indicated against each question in square brackets.

(c) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems

Q.1 In Fig.1, find the value of R_L for maximum power transfer across load. Also find the value of maximum power transfer through load resistance (R_L)

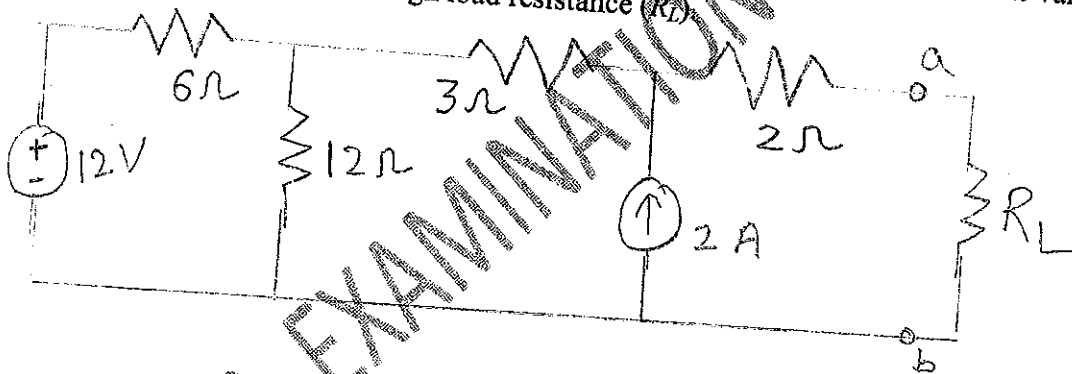


Fig.1

[CO1] [4Marks]

Q.2 Find the current flowing through 2Ω resistor in Fig.2 using superposition theorem.

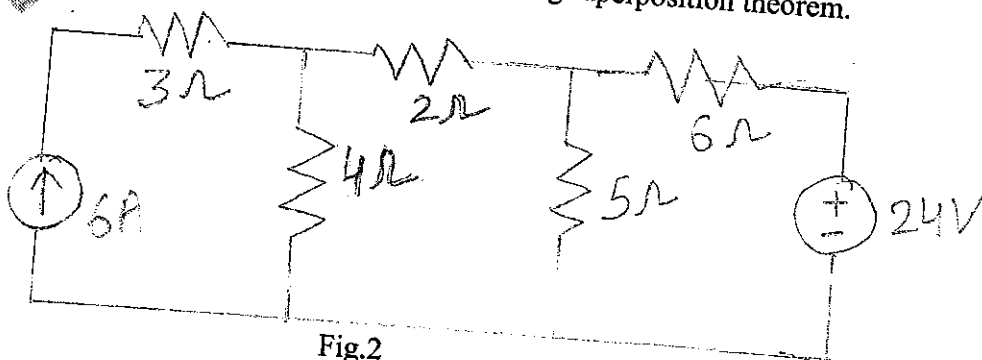


Fig.2

[CO1] [4Marks]

Q.3 Determine the equivalent input impedance across the terminal A and B in Fig.3. Assumed that the circuit operate at frequency $\omega=5$ rad/s. [CO2] [4Marks]

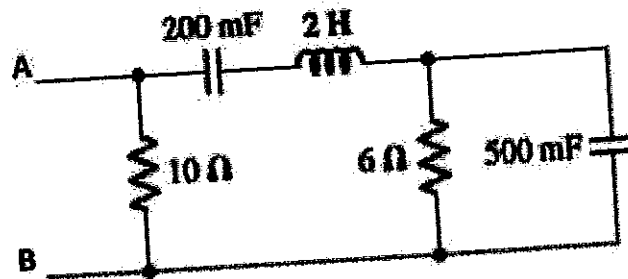


Fig.3

Q.4 Determine the v in the given figure (Fig.4) [CO1] [4Marks]

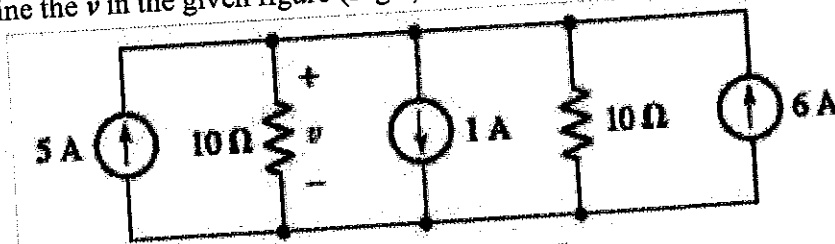


Fig.4

Q.5 The resistance of a coil is 3Ω and its time constant is 1.8 sec.. At $t=0$, a 10-V source is connected to it. Determine [CO2] [4 Marks]

- The current at $t=1$ sec.
- The time at which the current attains half of its final value
- The initial rate of growth of current.

Q.6 Determine the voltage $v(t)$ and $i(t)$ at $t=0^-$, 0^+ , and $t=0.05$ sec. for the circuit shown in given figure (Fig.5). [CO2,CO3] [5 Marks]

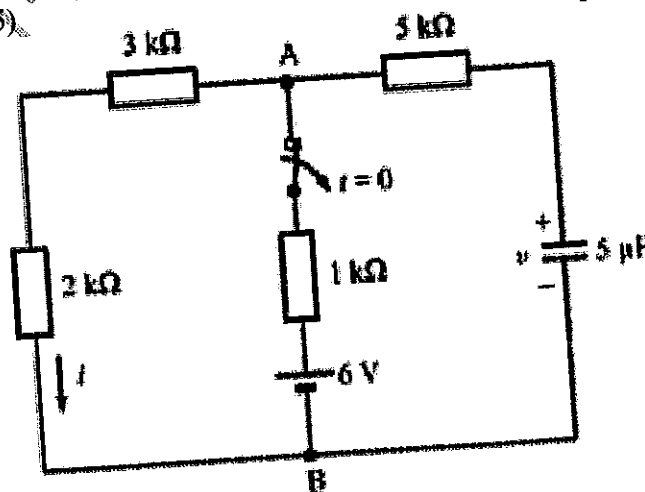


Fig. 5