

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -1 EXAMINATION- 2024

MSc-III Semester (Physics)

COURSE CODE(CREDITS): 24MS3PH301(3)

MAX. MARKS: 15

COURSE NAME: Electronics II

COURSE INSTRUCTORS: SKK

MAX. TIME: 1 Hour

*Note: (a) All questions are compulsory.*

*(b) Marks are indicated against each question in square brackets.*

1. Given the Logical Equation  $Y = (A + BC)(B + \bar{C}A)$ 
  - (a) Design circuit using basic logic gates.
  - (b) Is it possible to design circuit using NAND gate, If yes design the circuit.
  - (c) Simplify the equation.
  - (d) If the design is simplified, Design the circuit using NOR gates.
  - (e) Compare the three circuits in terms of no of inputs, no of gates and type of gates.

(1x5)
2. Minimize the four variable logic function using K-maps
  - (a)  $f(A, B, C, D) = \sum m(0,1,2,3,5,7,8,9,11,14)$  using SOP
  - (b)  $f(A, B, C, D) = \prod M(4,6,10,12,13,15)$  using POS
  - (c)  $f(A, B, C, D) = \sum m(0,3,5,6,9,10,12,15)$  using SOP

(1+1+1)
3. Implement the following multi output combinational logic circuit using a 4 to 16 line decoder
$$F1 = \sum m(1,2,4,7,8,11,12,13) \quad F2 = \sum m(2,3,9,11) \quad F3 = \sum m(10,12,13,14) \quad F4 = \sum m(2,4,8)$$

(2.5)
4. Carry is always there in full adder and half adder, How are they different in operations  

(2)
5. Design a 4 input logic circuit, having output as 1 only when any two inputs are 1. For all other conditions the output is 0  

(2.5)