

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -2 EXAMINATION- 2024

MSc -3rd Semester (Physics)

COURSE CODE (CREDITS): 24MS3PH301 (3)

MAX. MARKS: 25

COURSE NAME: Electronics-II

COURSE INSTRUCTORS: SKK

MAX. TIME: 1 Hour 30 Minutes

Note: (a) All questions are compulsory.

(b) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems

Q.No	Question	Marks
1	Define a 1-Bit memory cell and its working with block diagrams	3
2	Explain the minimization process of SOP and POS 2x2 K Maps with suitable examples	5
3	Differentiate between D-Type and T-Type flip-flop s with block diagrams and truth tables	4
4	Design a R-S flip flop with the following characteristic table	4


Characteristic table					Truth table for decoder	
CK	S	R	Q_n	Q_{n+1}	Y_1	Y_2
0	0	0	0	0	1	x
0	0	0	1	1	x	1
0	0	1	0	0	1	x
0	0	1	1	1	x	1
0	1	0	0	0	1	x
0	1	0	1	1	x	1
0	1	1	0	0	1	x
0	1	1	1	1	x	1
1	0	0	0	0	1	x
1	0	0	1	1	x	1
1	0	1	0	0	1	x
1	0	1	1	0	1	0
1	1	0	0	1	0	1
1	1	0	1	1	x	1
1	1	1	0	x	x	x
1	1	1	1	x	x	x

* $S = R = 1$ can happen with no clock.
** $S = R = 1$ must not happen.

5

Show that the circuit acts as bounce elimination switch

4

 

6

With the below mentioned clock (a) and input (b) are applied to D or J input of each of the following flip-flops, sketch the output wave form of the following

5

- i) Positive edge triggered D type flip flop 7474
- ii) Positive level triggered D type flip flop 7475
- iii) Negative edge triggered J-K flip flop(K=1) 74112
- iv) Master Slave J-K flip flop(K=1) 7476

