

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT  
 TEST -1 EXAMINATION- Feb 2018  
 B.Tech IV Semester(BI & BT)


COURSE CODE: 15B11EC411  
 COURSE NAME: Basic Electronics  
 COURSE CREDITS: 4

MAX. MARKS:15


MAX. TIME: One Hr

Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.

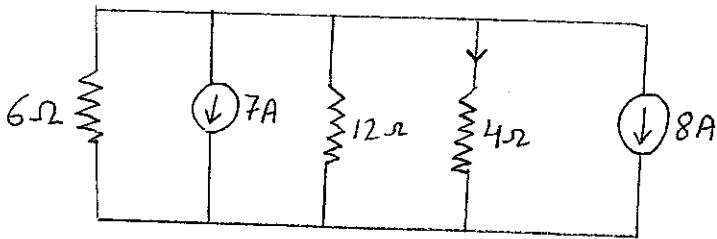
Q1) Using current divider technique, determine the current through the  $4\ \Omega$  resistance in the circuit of following figure. (4)



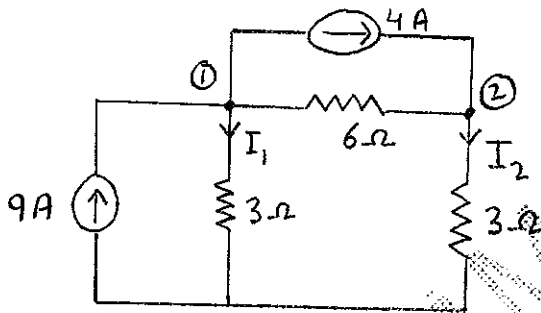Q2) Using nodal analysis to determine the current  $I_1$  and  $I_2$  (4)



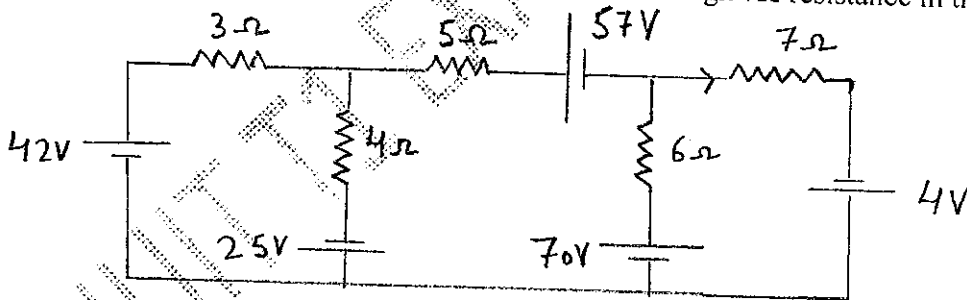Q3) Apply mesh analysis to determine current through  $7\ \Omega$  resistance in the network. (4)



Q4) Determine  $I$ ,  $I_1$ ,  $I_2$ ,  $V_{ab}$  and  $V_{bc}$  in the network of figure. (3)

