

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT
MID TERM (SUMMER SEMESTER EXAMINATION)- June-2018

COURSE CODE: 10B11EC211

MAX. MARKS:50

COURSE NAME: Basic Electronic Devices and Circuits


COURSE CREDITS: 4

MAX. TIME: 2 Hrs

Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.


- Q1. a)** Explain what is the reverse saturation current in a silicon diode and why it is much smaller than in a germanium diode.
(b) What is the difference between diffusion and drift current in P-n junction?
(c) How the characteristics of diodes change with the change in temperature?
(d) What are Figures of Merit of a Rectifier?
(e) The barrier potential developed across open-circuited PN-junction aids the flow of minority carriers from both sides of the junction. Explain how the current due to this flow of charge carriers is counter balanced. [10]

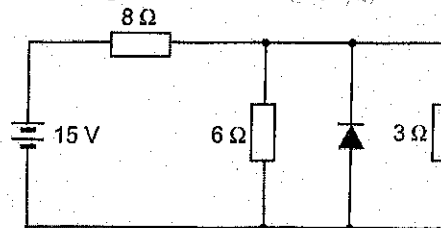- Q2. a)** Draw and explain VI characteristics of PN diode and give its characteristics equation
b) Determine the current through 3 ohm resistor, assume the diode be ideal. [6+4]



- Q3 a)** Differentiate between Zener and Avalanche Diodes and describe how Zener diode act as a voltage regulator.
(b) A zener regulator has input dc supply voltage of 25 V, a series resistance of 470 Ω, a zener voltage of 15 V, and a load resistance of 1 kΩ. What are the load voltage and the zener current? [6+4]

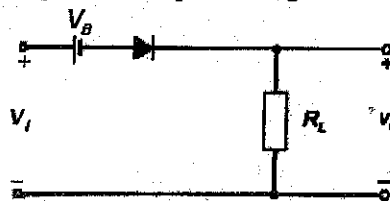- Q4. a)** What are Diode Clipper Circuits and biased clipper circuits? [6+4]
b) For the given circuit, find the output if the input voltage is 15 V sinusoidal signal.



- Q5. a)** Explain Full wave Rectifier and calculate its Ripple factor. [6+4]