

Dr. Prayag

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST 3 EXAMINATIONS – MAY 2018

B.Tech IInd Semester (ECE/CSE/IT)

COURSE CODE: 10B11EC211

MAX. MARKS: 35

COURSE NAME: Basic Electronic Devices and Circuits

COURSE CREDITS: 04

MAX. TIME: 2 HRS


Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means. Assume any missing data.

Q1.


[3+3+3]

(a) Differentiate between conductors, insulators and semiconductors on the basis of energy band diagram. [CO1]

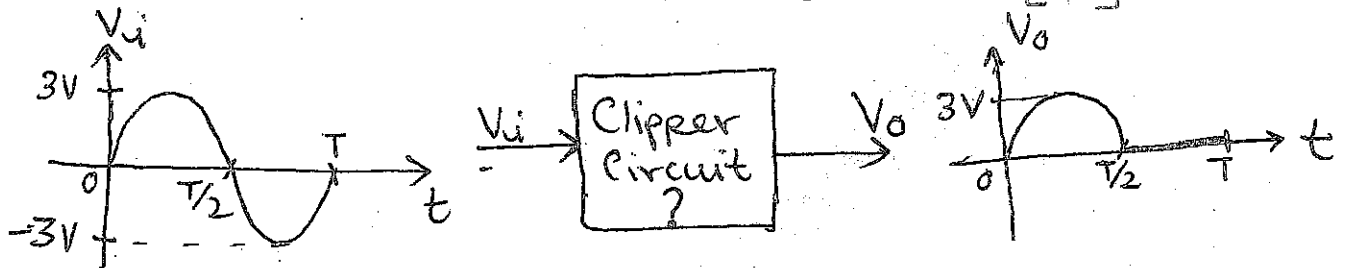(b) Design a clipper circuit for the following input and output waveforms: [05]



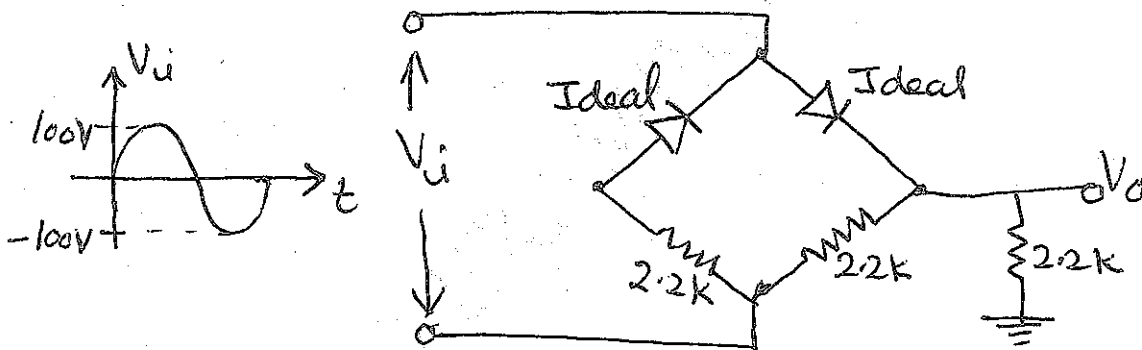
(c) Explain the working of the circuit given below and sketch the output (V_o) waveform. [04]



Q2.

[3+3+3]

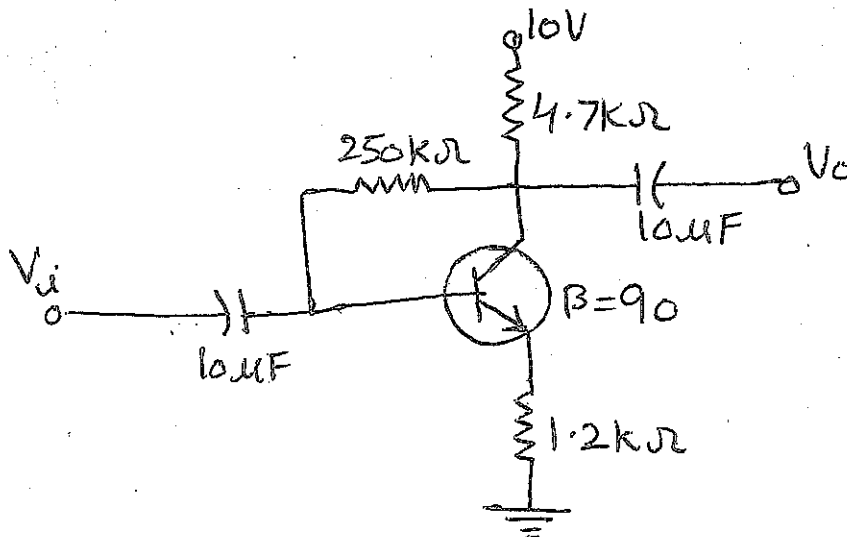(a) Determine I_{CQ} and V_{CEQ} for the following network: [03]



(b) Draw the fixed bias configuration for npn BJT and derive the expression for the quiescent current and voltage. [C03]

(c) Draw the fully labeled input and output characteristics for common emitter npn BJT. [C02]

Q3.

[4+2+3]

(a) Draw the construction of n-channel JFET and explain its working. Also define pinch-off voltage. [C02]

(b) Differentiate between the enhancement and depletion type MOSFET on the basis of construction. [C02]

(c) Draw the transfer characteristics of n-channel JFET defined by $I_{DSS} = 12 \text{ mA}$ and $|V_p| = 6 \text{ V}$. [C02]

Q4.

[2+3+3]

(a) Write down the characteristics of ideal operational amplifier. [C04]

(b) Draw the circuit diagram of subtractor circuit using OP-AMP and show that the output voltage is proportional to the difference of two inputs. [C05]

(c) For the given three stage amplifier circuit determine the value of output voltage: [C05]

