

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT  
 MID SEMESTER EXAMINATION (SUMMER SEMESTER)(II<sup>ND</sup> SEMESTER BT)

COURSE CODE: 15B11EC411

MAX. MARKS: 50

COURSE NAME: BASIC ELECTRONICS

MAX. TIME: 2 HRS.

Note: All questions are compulsory. Carrying of mobile phone during examination will be treated as case of unfair means. Use of calculator is permitted.

Q1 (a) Determine the total resistance between points A and B in the network shown in Fig. 1. [5 Marks]

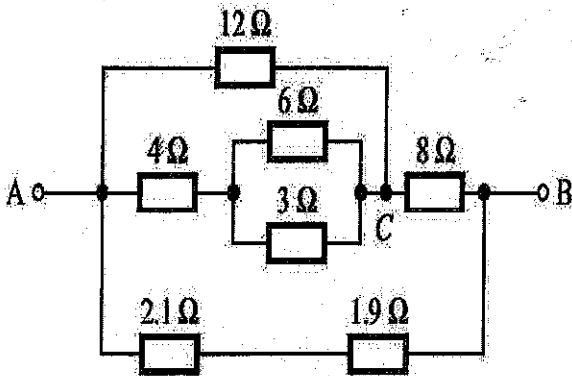


Fig. 1

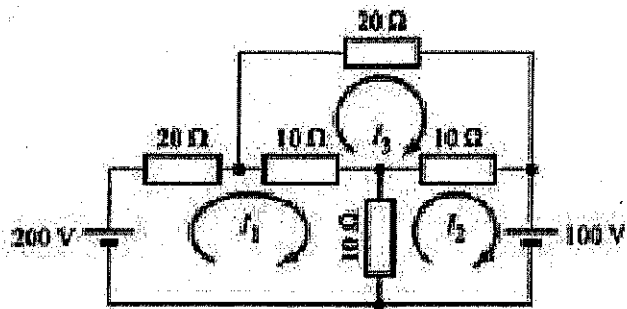


Fig. 2

(b) A 10-Ω resistance is in series with a parallel combination of 15-Ω resistance and 5-Ω resistance. If the current in 5-Ω resistance is 6 A, what total power is dissipated in the three resistances? [5 Marks]

Q2 (a) Explain the working of a full wave bridge rectifier in detail with the input and output waveforms. [7 Marks]

(b) How does a BJT work in common emitter mode. Describe the input and output characteristics. [8 Marks]

Q3(a) With the help of a suitable diagram differentiate between the two types of transistor. [7 Marks]

(b) What is the affect of biasing on the depletion region of a PN diode. Explain in detail. [8 Marks]

Q4(a) Apply mesh analysis and determine the loop currents  $I_1$ ,  $I_2$  and  $I_3$  in the Fig 2. [5 Marks]

(b) Why is common collector configuration required? Write the expression for  $\alpha$  for CB configuration. [5 Marks]

\*\*\*\*\*