

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -2 EXAMINATION- 2025

B.Tech-II Semester (CSE/IT, ECE, CE)

COURSE CODE(CREDITS): 24B11EC211(4)




MAX. MARKS: 25





COURSE NAME: Basic Electrical Engineering

COURSE INSTRUCTORS: RKU, HSL, SWT, NTJ, PRG, SRU

MAX. TIME: 1 hr 30 min

Note: (a) All questions are compulsory. (b) The candidate is allowed to make suitable numeric assumptions wherever required for solving problems.

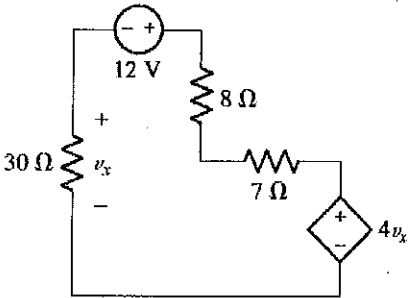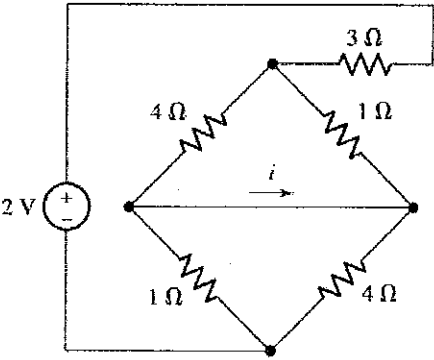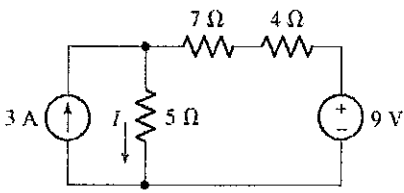Q.No	Question	CO	Marks
Q.1	<p>(a) Find the power absorbed by the $7\ \Omega$ in the circuit.</p>  <p>(b) Employ any method/procedure of your choice to obtain a value for the current labeled i in the circuit below.</p> 	CO-1	2+3
Q.2	<p>(a) State the Superposition Theorem. What is the main condition for applying Superposition Theorem in an electrical circuit?</p> <p>(b) Using superposition, determine the current I in the circuit.</p> 	CO-2	2+3

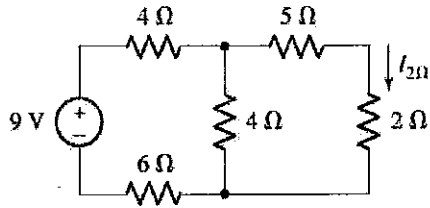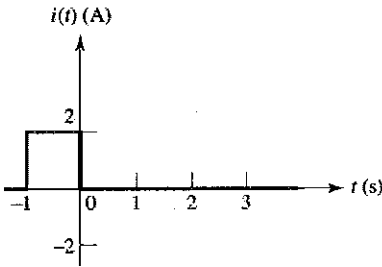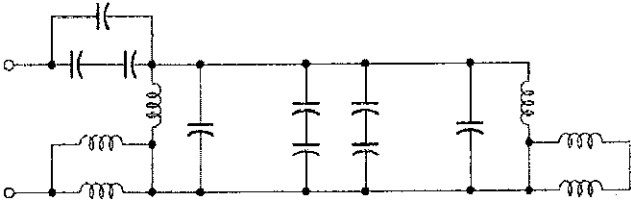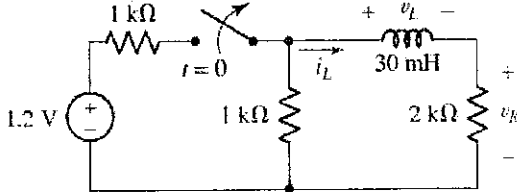Q.No	Question	CO	Marks
Q.3	<p>(a) Use Thevenin's theorem to find the current through the $2\ \Omega$ resistor in the circuit below.</p>  <p>(b) Assuming the $2\ \Omega$ resistor in the above circuit as the load resistor (R_L), determine the new value of R_L required for maximum power transfer. Also, calculate the maximum power delivered to this new load resistor.</p>	CO-2	3+2
Q.4	<p>(a) Assuming the passive sign convention, sketch the voltage which develops across the terminals of a $2.5\ \text{F}$ capacitor in response to the current waveform given below.</p>  <p>(b) Reduce the network given below to the smallest possible number of components if each inductor is $1\ \text{nH}$ and each capacitor is $1\ \text{mF}$.</p> 	CO-3	2+3
Q.5	<p>The switch shown in circuit below has been closed for 6 years prior to being flipped open at $t = 0$. Determine i_L, v_L, and v_R at t equal to (a) 0^-; (b) 0^+; (c) $1\ \mu\text{s}$; (d) $10\ \mu\text{s}$.</p> 	CO-3	5