

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -2 EXAMINATION- 2025

B.Tech-II Semester (CSE/IT/ECE/CE/BT/B1)

COURSE CODE (CREDITS): 18B11EC211(4)

MAX. MARKS: 25



COURSE NAME: Electrical Sciences

COURSE INSTRUCTORS: Prof. Rajiv Kumar, Dr. Harsh Sohal, Dr. Shweta Pandit, Dr. Salman Raju, Dr. Nishant Jain and Lt. Pragya Gupta

MAX. TIME: 1 Hour 30 Min

Note: (a) All questions are compulsory.

(b) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems

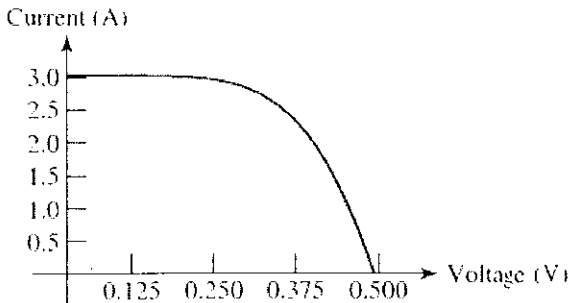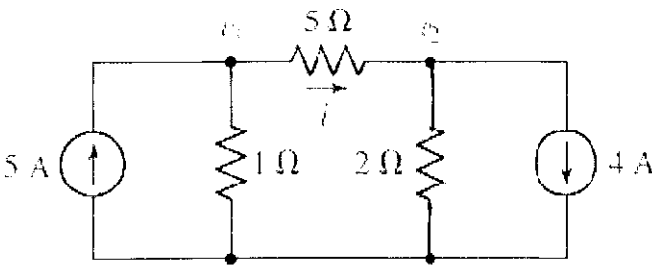Q.No.	Question	CO	Marks
Q1	<p>The current-voltage characteristic of a silicon solar cell exposed to direct sunlight at noon in Florida during midsummer is given in Fig. 1. It is obtained by placing different-sized resistors across the two terminals of the device and measuring the resulting currents and voltages. (a) What is the value of the short-circuit current? (b) What is the value of the voltage at open circuit? (c) Estimate the maximum power that can be obtained from the device.</p>  <p style="text-align: center;">Fig.1</p>	CO2	5
Q2	<p>(a) Write nodal equations for the circuit below. (b) Write mesh equations for the same circuit.</p>  <p style="text-align: center;">Fig. 2</p>	CO3	2.5-2.5

- Q3 (a) Explain superposition theorem with respect to circuit analysis with the help of an example.
 (b) Considering the circuit of Fig. 3, employ superposition to determine the two components of i_8 arising from the action of the two independent sources, respectively.

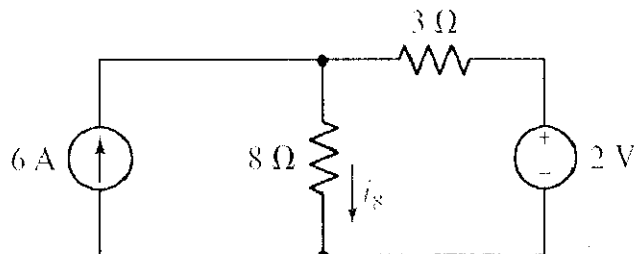


Fig. 3.

- Q4 Referring to Fig. 4, (a) determine the Thevenin equivalent of the network connected to R_L .
 (b) Determine v_L for $R_L = 1\ \Omega, 3.5\ \Omega, 6.257\ \Omega$, and $9.8\ \Omega$.

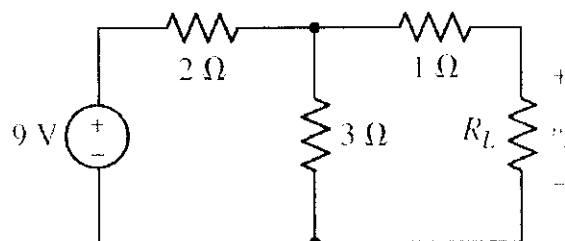


Fig. 4.

- Q5 For the circuit of Fig. 5 below find the voltage labeled v at $t = 200$ ms. The switch is opened at $t = 0$.

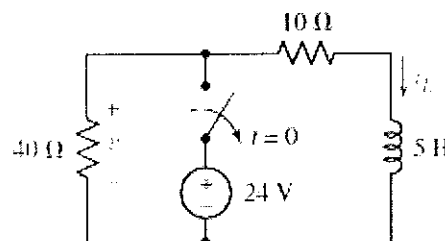


Fig. 5.