

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -3 EXAMINATION- MAY-2025

B.Tech-IV Semester (ECE)

COURSE CODE(CREDITS): 18B11EC411 (03)

MAX. MARKS: 35

COURSE NAME: ANALOG INTEGRATED CIRCUITS

COURSE INSTRUCTORS: Dr. Shruti Jain

MAX. TIME: 2 Hours

Note: (a) All questions are compulsory.

(b) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems

Q.No	Question	CO	Marks
Q1	i. In which mode 555 timer can be used as a frequency divider.	CO2	5
	ii. Which component is essential in a clamper circuit for maintaining the shifted voltage level?		
	iii. Which pin of the 555 timer is used to reset the timer?		
	iv. Which op-amp configuration is most commonly used in weighted resistor DACs? (inverting summing amplifier / non-inverting summing amplifier)		
	v. Which op-amp-based ADC method uses an integrator and a comparator?		
Q2	i. Design a clipper circuit using an op-amp that clips the output signal at +2V and -2V.	CO2	3 + 2
	ii. Design a clamper using an op-amp that adds a DC bias of +5V to an AC signal.		
Q3	Compare a comparator and a Schmitt trigger. When would you use one over the other?	CO2	5
Q4	A 555 timer is configured in astable mode to generate a square wave signal. The circuit uses two resistors, R_1 and R_2 , and a capacitor C . The supply voltage V_{CC} is 9V. The output waveform needs to have a frequency of approximately 1 kHz and a duty cycle of 60%.	CO3	2.5 + 2.5
	i. Explain the working principle of the 555 timer in astable mode, specifically detailing the function of the threshold,		

	trigger, and discharge pins during the charging and discharging cycles of the capacitor.		
	ii. Design the circuit.		
Q5	i. Describe the working of an R-2R ladder DAC with an op-amp. How does an op-amp improve the output of a DAC? ii. Why is the op-amp in an inverting configuration in most DAC designs?	CO3	3 + 2
	i. What is an oscillator? What conditions must be met for sustained oscillation in an op-amp circuit?		
Q6	ii. What is the Barkhausen criterion? Name two types of op-amp-based oscillators. What is the function of the feedback network in an oscillator?	CO4	2.5 + 2.5
	i. Define capture range and lock range in a PLL. How are they different?		
Q7	ii. What is the role of the voltage-controlled oscillator in a PLL? iii. List at least three practical applications of PLLs in communication systems.	CO5	2 + 2 + 1