

**JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT**

**TEST -3 EXAMINATION- May 2018**

**B.Tech VI Semester**

COURSE CODE: 10B11EC612

MAX. MARKS: 35

COURSE NAME: VLSI TECHNOLOGY AND APPLICATIONS

COURSE CREDITS: 04

MAX. TIME: 2 Hrs

*Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.*

1. [CO1, CO2, CO3, CO4, CO5][1 \* 10 =10]
- I. Show analytically by using equations how the gate capacitance is affected in terms of scaling factor  $S$  using full scaling method.
  - II. Specify the colors for  $n$ -diffusion, metal 1 layer, polysilicon and demarcation line in stick diagram.
  - III. Find the region of operation for the MOSFET working with following parameters:  
 $V_G = -1V$ ,  $V_S = 2V$ ,  $V_D = -3V$ ,  $V_{th} = -1.5V$ ?
  - IV. In general,  $p$ -MOS in series implement a \_\_\_\_\_ gate. How many  $n$ -MOS transistors are in logic diagram of NAND 3 gate?
  - V. Does the substrate bias effect, affect CMOS circuits? How.
  - VI. What is the formula for  $C_{GD}$  and  $C_{GB}$  in saturation region for oxide related capacitance? Assume overlap length.
  - VII. If  $V_{OH} = 4.5V$ ,  $V_{OL} = 0.3V$ ,  $\gamma = 0.38V^{1/2}$  and  $|2\phi_f| = 0.6V$ . Find the threshold voltage for load assuming this value is used in calculation of  $V_{IL}$ . Assume  $V_{TO} = 0.8V$ .
  - VIII. Give the formula for voltage equivalence factor ( $K_{eq}$ ) and zero bias capacitance ( $C_{j0}$ ).
  - IX. Find  $i$  as a function of  $v$  for the circuit shown in Fig 1 for linear and saturation region. Neglect the effect of  $\lambda$  on  $v_{DS} - i_D$  in the saturation region.

 


Fig 1

X. Assuming linear load, draw the logic diagram for  $\overline{AB+CD}$ .

2. A NOR3 gate uses identical  $n$ -MOS and  $p$ -MOS with an aspect ratio of 4 for each MOS. The  $n$ -MOS process trans-conductance is  $120\mu\text{A}/\text{V}^2$ , and the threshold voltage of  $0.55\text{V}$ . A power supply of  $5\text{V}$  is chosen for the circuit. Find the value of  $p$ -MOS process trans-conductance needed to create a gate where the case of simultaneous switching gives the midpoint of  $2.4\text{V}$ . Assume  $V_{tp} = -0.9\text{V}$ . [CO1, CO4] [5]

3. For the CMOS inverter  $V_{Tn} = 0.5\text{V}$ ,  $V_{Tp} = -0.5\text{V}$ ,  $k_n' = 80\mu\text{A}/\text{V}^2$ ,  $k_p' = 40\mu\text{A}/\text{V}^2$  and  $V_{DD} = 3.3\text{V}$ ,  $(W/L)_n = (W/L)_p = 4$ .

- Find the transition points for the  $p$ -MOS and  $n$ -MOS.
- Find  $v_i$ , when  $v_o = 0.5\text{V}$
- Find  $v_i$  when  $v_o = 2.8\text{V}$
- Give the conditions for Symmetric CMOS inverter.

[CO4] [2 + 1.5 + 1.5 + 1 = 6]

4. Explain the different steps of fabrication for enhancement  $n$ -type IGFET. [CO5] [5]

5. Draw the stick diagram of the logic expression  $f(A, B, C) = \overline{A(B+C)(A+B)}$  using CMOS logic. Find the equivalent CMOS inverter circuit for simultaneous switching of all input, assuming that  $(W/L)_n = 15$  for all  $n$ -MOS transistor and  $(W/L)_p = 20$  for all  $p$ -MOS transistor. [CO5] [5]

6. What are pass transistors? Derive *pull up to pull down* ratio if one of the inverter is fed to another inverter through a series of three pass transistors. Assume  $V_{th} = 0.2V_{DD}$ ,  $V_{thdep} = -0.6V_{DD}$  and  $V_{thp} = 0.3V_{DD}$ . [CO6][1 + 3 = 4]