

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -2 EXAMINATION- 2025

B.Tech-I Semester (BT/BI)

COURSE CODE (CREDITS): 25B11EC112





MAX. MARKS: 25


COURSE NAME: BASIC ELECTRONICS FOR LIFE SCIENCES

COURSE INSTRUCTORS: Er. Munish Sood

MAX. TIME: 1 Hour 30 Min

- Note:** (a) All questions are compulsory.
 (b) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems.
 (c) Scientific calculator is allowed.

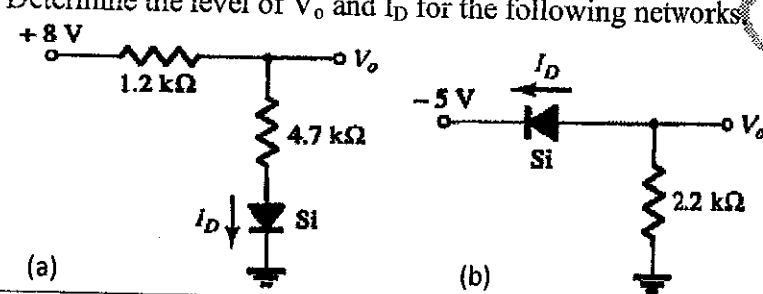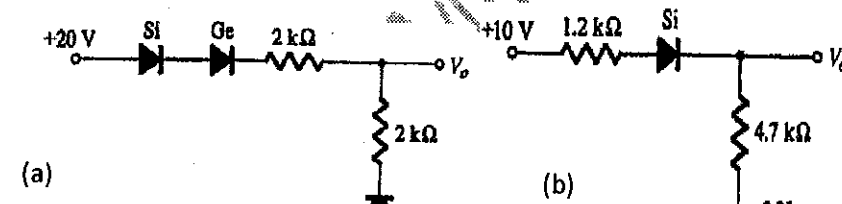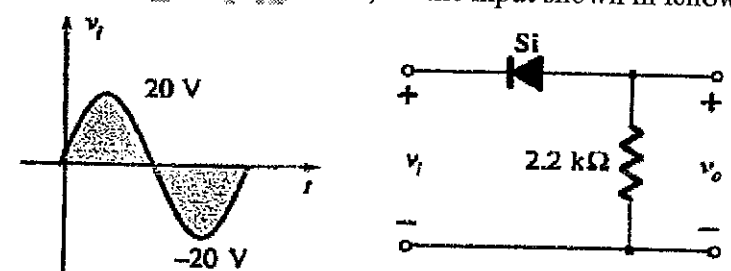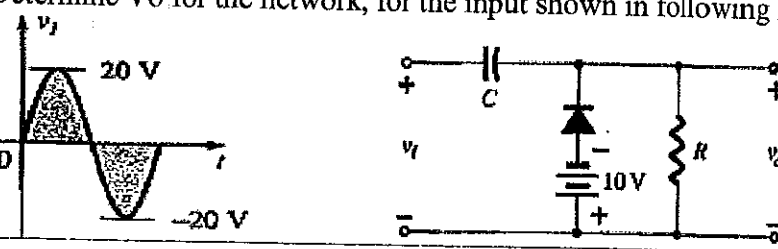Q.No	Question	CO	Marks
Q1	Determine the level of V_o and I_D for the following networks 	2	4
Q2	Determine the level of V_o for the networks. 	2	4
Q3)	Determine V_o for the network, for the input shown in following figure. 	3	4
Q4)	Determine V_o for the network, for the input shown in following figure. 	3	4

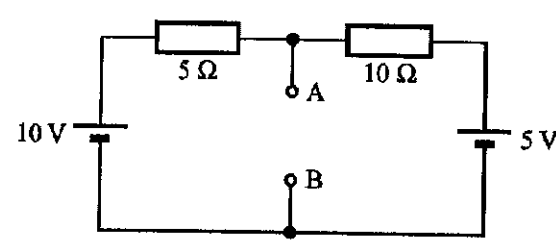Q5)	<p>Obtain the Norton's equivalent circuit with respect to the terminals AB for the network shown, and hence determine the value of the current that would flow through a load resistor of $5\ \Omega$ if it were connected across terminals AB.</p> 	1	5
Q6)	<p>a) Illustrate two applications of the transistor? b) What are three modes of operation of the BJT? c) What are the two types of transistor? d) Name the three terminals of a transistor?</p>	2	4

JUT TEST-2 EXAMINATION - OCT 2025