

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST-2 EXAMINATION-OCTOBER-2025

B.Tech-IIIrd Semester (ECE/ECS/EE, Minor Degree)

COURSE CODE (CREDITS): 25B11EC312/18B11EC312 (4)

MAX. MARKS: 25

COURSE NAME: Digital Circuit Design/Digital Circuit & Logic Design

COURSE INSTRUCTOR: Dr. Pardeep Garg

MAX. TIME: 1.5 Hours

Note: (a) All questions are compulsory. (b) The candidate is allowed to make suitable numeric assumptions wherever required for solving problems.

Q.No	Question	CO	Marks
Q1	Design a 1-bit magnitude comparator using a 2-to-4 line decoder. Clearly show how the decoder outputs can be combined to generate the three comparator conditions.	CO-3	3
Q2	Design 2-input NOR, and XOR gates using suitable multiplexer (show output for each case separately).	CO-3	2
Q3	An air-conditioning unit is controlled by four variables: temperature T, humidity H, the time of the day D, and the day of the week W. The unit is turned on under any of the following circumstances: - The temperature exceeds 78°F, and the time of the day is between 8 a.m. and 5 p.m. - The humidity exceeds 85%, the temperature exceeds 78°F, and the time of day is between 8 a.m. and 5 p.m. - The humidity exceeds 85%, the temperature exceeds 78°F, and it is a weekend. - It is Saturday or Sunday and humidity exceeds 85%. Write a logic expression for controlling the air-conditioning unit. Simplify the expression obtained as far as possible.	CO-3	3.5
Q4	A priority encoder with 4 decimal inputs (D {MSD}, C, B, and A {LSD}) where D is having the lowest priority and A is having the highest priority has to be designed. Obtain the truth table for it.	CO-3	2
Q5	Design and discuss the functioning of a 4-bit binary parallel adder-subtractor circuit (in one circuit) that can perform both addition and subtraction (using Complement's method) of two 4-bit unsigned binary numbers, $A = A_3A_2A_1A_0$ and $B = B_3B_2B_1B_0$.	CO-3	2.5
Q6	Design a 32:1 multiplexer using 8:1 multiplexers (all having active-high enable input) & 2:4 decoder (all in one-circuit only).	CO-3	4.5
Q7	A combinational circuit has to be designed for the following situation: The input should be 4-bit binary number and the output should be the 2's complement of the input. i) Obtain the truth-table for it.	CO-3	1.5+1.5 = 3

	ii) Obtain the Boolean expression of the output variables.		
Q8	What is a demultiplexer? Discuss its basic functioning along with one practical application.	CO-3	2.5
Q9	Differentiate between combinational and sequential circuits.	CO-4	2

JUT TEST-2 EXAMINATION-OCTOBER-2025