

Dr Manakshi

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT
TEST -3 EXAMINATION- December-2018
B.Tech III Semester

COURSE CODE: 10B11EC401
 COURSE NAME: DIGITAL ELECTRONICS
 COURSE CREDITS: 04

MAX. MARKS: 35

MAX. TIME: Two Hours

Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.

- Differentiate between Moore and Mealy machines
 - What is race around condition? How is it eliminated?
 - Convert decimal 2142 in BCD

[CO2] [3]
- A sequential circuit uses two JK flip-flops as memory elements. The behavior of the circuit is described by the following equations:

$$J_A = B, K_A = \bar{X}, J_B = \bar{X}.B, K_B = A \oplus X, Y = A \oplus B$$

Derive the state table and draw the state diagram of the circuit.

[CO3] [7]
- Draw the logic diagram of a four bit register with four D flip flops and four 4:1 multiplexers with mode selection inputs s_1 and s_0 . The register operates

[CO4] [5]

S_1	S_0	Register Operation
0	0	No change
0	1	Complement the four outputs
1	0	Clear register to 0 (synchronous with the clock)
1	1	Load parallel data

- Design a sequential circuit using D flip flop that goes through states 0, 1, 2, 4, 0. The undesired (unused) states must always go to zero (000) on the next clock pulse.

[CO4] [5]
- Draw the logic diagram of a MOD – 10 count up Ripple counter
 - Design a circuit which will convert an S-R flip flop to JK flip flop

[CO5] [2.5]
[2.5]
- Design a circuit which detects the decimal numbers 4 through 11 in 4 bit binary code input using AOI logic. Give any two applications of the circuit.

[CO6] [5]
- For the given multiplexer, derive the Boolean expression and realize it with any universal gate.

[CO6] [5]

