

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT
 TEST -II EXAMINATION- Oct 2018
 B.Tech. III Semester (ECE)

COURSE CODE: 10B11EC312
 COURSE NAME: Analog Electronics
 COURSE CREDITS: 4

MAX. MARKS: 25

MAX. TIME: 1 Hr 30 Min

Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.

Q1) For the network of Fig.1 determine r_e , V_B , V_C , Z_i and A_{VNL} .

 


Fig.1

(5)

Q2) Calculate the voltage gain of each stage and the overall ac voltage gain for the BJT cascade amplifier circuit of Fig.2.


 
 


Fig.2

(5)

 Q3) Determine Z_i , Z_o and A_v for the network of Fig.3 if $I_{DSS} = 10\text{mA}$, $V_P = -4\text{V}$, and $r_d = 40\text{K}\Omega$. (5)



Q4) Determine V_o for the network of Fig.4 if $V_i = 4\text{mV}$, $I_{D(on)} = 4\text{mA}$ and $V_{GS(on)} = 7\text{V}$. (5)

Q5) For the self Bias JFET network of Fig. 5. Determine A_{vNL} , Z_i and Z_o and A_{vS} (voltage gain with source resistance and load resistance) (5)

