

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT
 TEST -3 EXAMINATION- Dec 2018
 B.Tech III Semester

COURSE CODE: 10B11EC312
 COURSE NAME: Analog Electronics
 COURSE CREDITS: 3


MAX. MARKS: 35

MAX. TIME: 2 Hrs

Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.


Q1) Determine the lower cut off frequency for the network of following Fig.1. $C_G=0.01\mu\text{F}$, $C_C = 0.5\mu\text{F}$, $C_S = 2\mu\text{F}$, $R_{\text{SIG}} = 10\text{K}\Omega$, $R_G = 1\text{M}\Omega$, $R_D = 4.7\text{k}\Omega$, $R_S = 1\text{k}\Omega$, $R_L = 2.2\text{k}\Omega$, $I_{\text{DSS}} = 8\text{mA}$, $V_P = -4\text{V}$, $r_d = \infty\Omega$, $V_{\text{DD}} = 20\text{V}$ (5)

Fig. 1

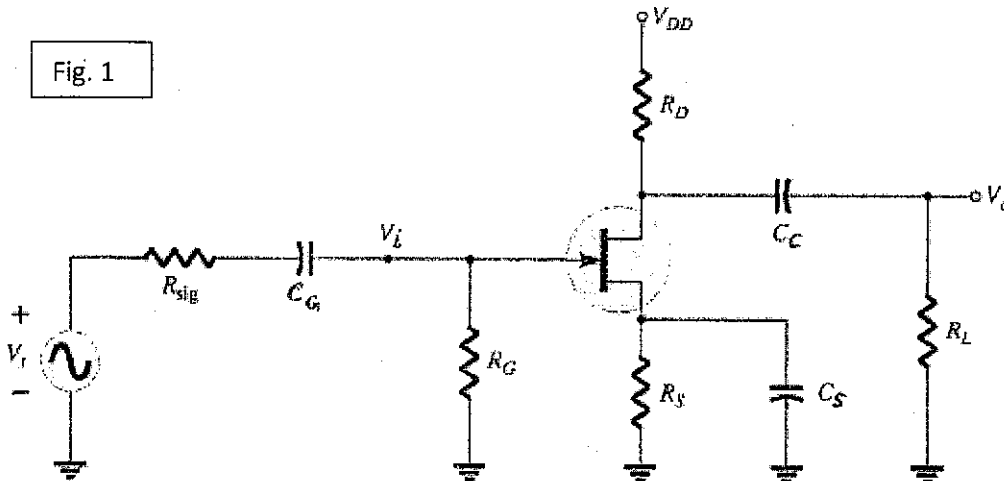

Q2) Determine the upper cut off frequency f_{Hi} and f_{Hlo} for the network of Fig. 2. With $R_S = 1\text{k}\Omega$, $R_1 = 40\text{k}\Omega$, $R_2 = 10\text{k}\Omega$, $R_E = 2\text{k}\Omega$, $R_C = 4\text{k}\Omega$, $R_L = 2.2\text{k}\Omega$, $\beta = 100$, $r_o = \infty$, $V_{\text{CC}} = 20\text{V}$. $C_{\text{be}} = 36\text{pF}$, $C_{\text{bc}} = 4\text{pF}$, $C_{\text{ce}} = 1\text{pF}$, $C_{\text{Wi}} = 6\text{pF}$, $C_{\text{Wo}} = 8\text{pF}$. (5)


Fig. 2

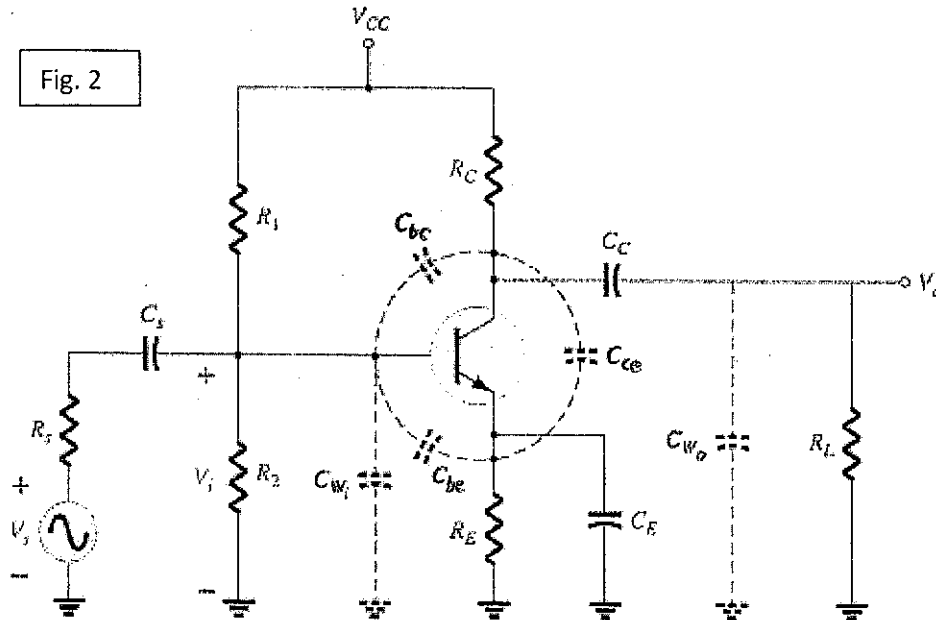

Q3) What is Barkhausen criteria for oscillators ? Derive the expression for frequency of oscillation for RC phase shift oscillator. (5)

Q4) Calculate the gain without and with feedback for the network of Fig. 3. (Using voltage series feedback) with $\beta = 210$ and $r_o = 50 \text{ k}\Omega$ (5)

Fig. 3

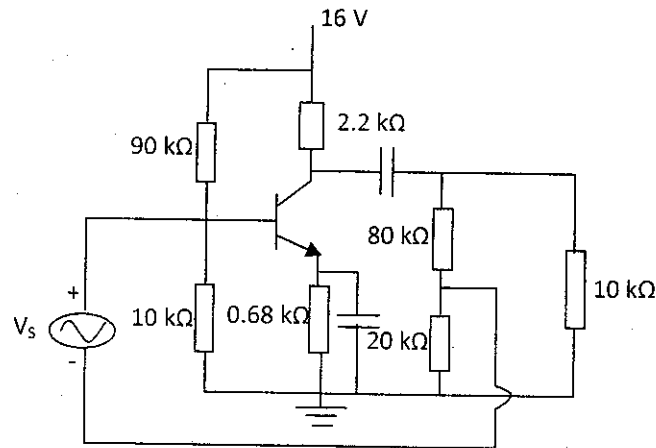

Q5) Calculate the no load voltage gain for the cascode configuration of Fig.4 (5)

Fig. 4


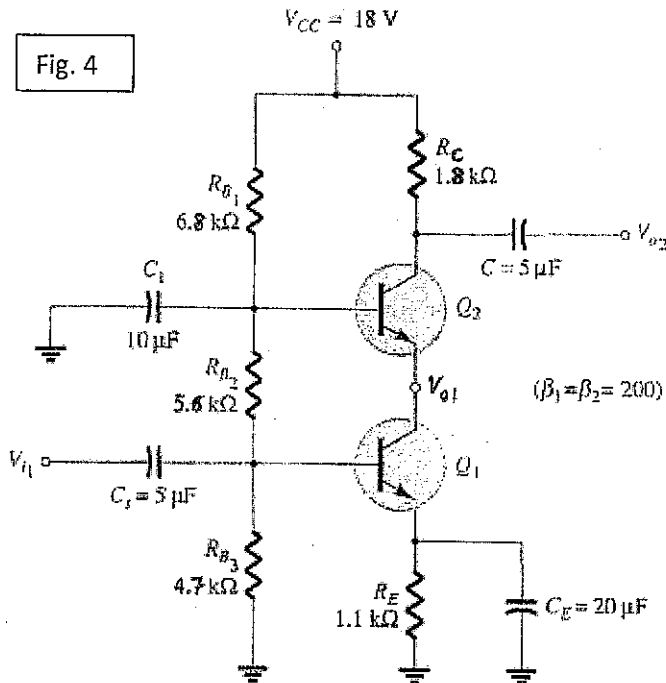


Fig. 5

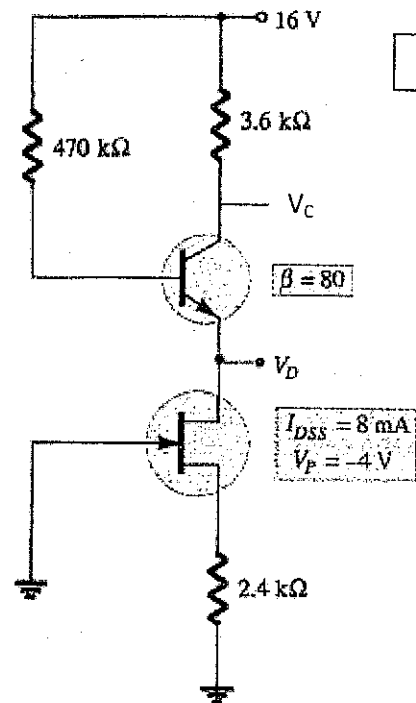

Q6) Determine V_D and V_C for the network of Fig. 5. (5)

Q7)

- a) What turns ratio transformer is needed to couple an 8Ω load so that it appears as an $8 \text{ k}\Omega$ effective load? (5)
- b) Draw the circuit diagram and explain the working of a class B npn push-pull power amplifier using transformer coupled input. (5)