

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -2 EXAMINATION- October 2017

B.Tech (ECE) 3rd Semester

COURSE CODE: 10B11EC312

MAX. MARKS: 25


COURSE NAME: Analog Electronics

COURSE CREDITS: 4

MAX. TIME: 1.5 Hrs

Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.

 Q1- For the given Darlington transistor draw the ac equivalent circuit, r_e model and Calculate the voltage gain. Repeat the problem if a resistor $R_c = 200K\Omega$ is added along with a bypass capacitor C_E . Output is now off the collector of the transistor. In both the cases ignore r_o . [6]



Q2- (a) Draw the neat circuit diagram of Emitter follower and show that in emitter follower $A_V = 1$. Ignore r_o . [4]

(b) Given $h_{ie} = 2.2K\Omega$, $h_{fe} = 100$, $h_{re} = 4 \times 10^{-4}$, and $h_{oe} = 25\mu S$, draw the following:

- i. Common Emitter hybrid equivalent model.
- ii. Common Emitter r_e equivalent model
- iii. Common base hybrid equivalent model
- iv. Common base r_e equivalent model

[2]

Q3- For voltage divider bias circuit with bypass capacitor C_E , prove that $A_{VNL} > A_{VL} > A_{VS}$. Ignore r_o . [6]

Q4- For the given cascade system with two identical stages, determine:

- a. The loaded voltage of each stage.
- b. The total ~~voltage~~ gain of the system (A_{VS})
- c. The loaded current gain of each stage.
- d. The total current gain of the system
- e. How Z_i is affected by the second stage and R_L ?
- f. How Z_o is affected by the first stage and R_s
- g. The phase relationship between V_o and V_i .

[7]

