

Vikar Bahgal

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST-2 EXAMINATION- APRIL - 2019

B. Tech (2nd Semester) (ECE/CSE/IT/CE)

COURSE CODE: 18B11EC211

MAX. MARKS: 25

COURSE NAME: ELECTRICAL SCIENCES


COURSE CREDITS: 04

MAX. TIME: 1.5 HR

Note: All questions are compulsory. Carrying of mobile phone during examination will be treated as case of unfair means. Marks are indicated below each question


Q1. a) Find equivalent resistance between terminals A & B.

[2.5] CO1

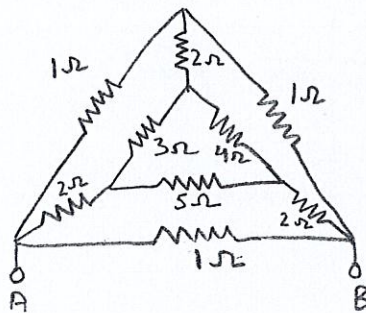


b) Find node voltages for given circuit.

[2.5]

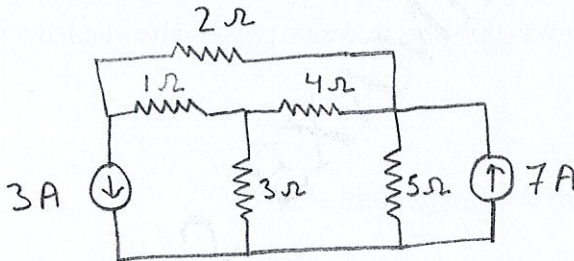


Q2. For the given circuit find current $i_L(t)$ at time (a) $t = -1$ s, (b) $t = 0$ s and (c) $t = 5$ ms.

[5] CO4

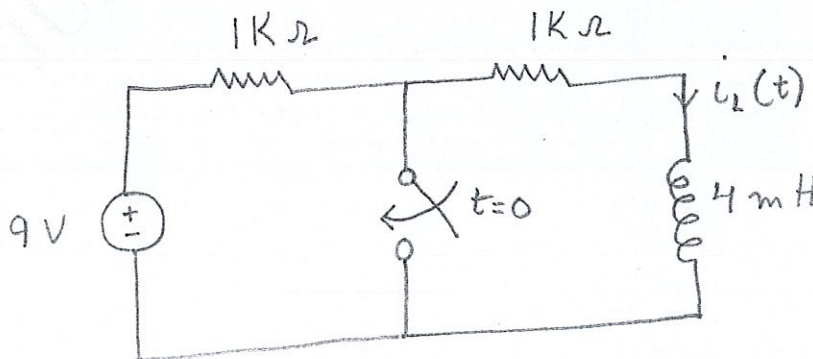


Q3. Find the equivalent impedance Z_{eq} between terminals A & B.

[5] CO1

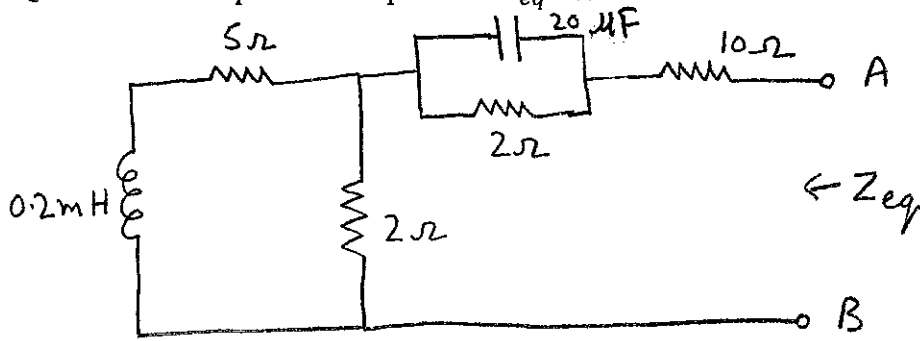

Q4. Find the current $i(t)$ in the following circuit.

[5] CO4

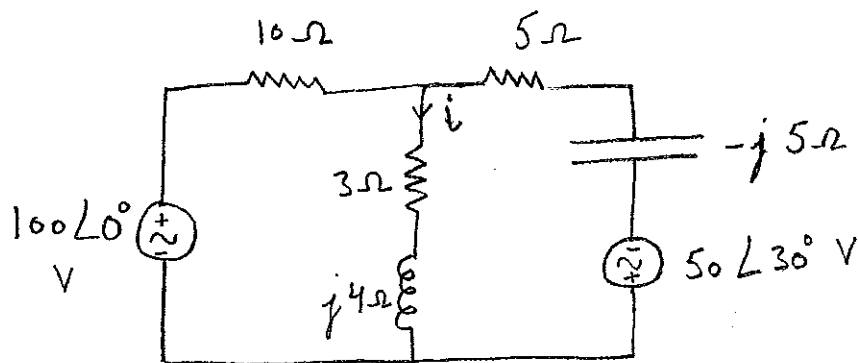

Q5. (a) Derive Average power for given voltage $v(t) = V_m \sin(\omega t + \theta)$ and current $i(t) = I_m \sin(\omega t + \phi)$. And also prove that the average power absorbed by pure reactive load is zero.

[4] CO4

(b) Calculate rms value of current $i(t) = 5 \cos(200\pi t - 30^\circ)$.

[1]