

Harsh Sohel

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST-2-EXAMINATION – April 2019

B.Tech., IInd Semester, BT-BI

COURSE CODE: 18B11EC212

MAX. MARKS: 25

COURSE NAME: BASIC ELECTRICAL SCIENCE


COURSE CREDITS: 4

MAX. TIME: 1:30 Hr.

Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means. Missing data, if any, can be appropriately assumed.

Q1. [CO1]

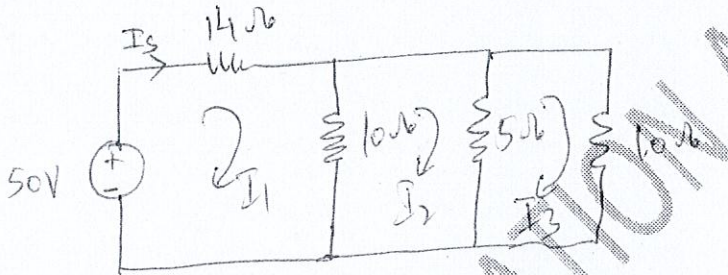- (i) Why RC circuit is a better choice in making timer circuits? (1)
- (ii) Capacitance (C) is a dual of Inductance (L). Explain. (1)
- (iii) Explain the concept of duality in electrical circuits with reference to Thevenin's and Norton's theorem. (3)
- (iii) Apply mesh analysis to determine current drawn from the source in the network of Fig. given below. (2)



Q2. [CO2, CO3]

- (i) An alternating current of frequency 50 Hz has a maximum value of 13 A. (a) Write down the equation for its instantaneous value. (b) Find the value of current after 1/360 seconds (c) Find the time taken to reach 9.6A for the first time. (3)
- (ii) Determine the *average* and *rms* value of resultant current in a wire carrying simultaneously a dc current of 5A and a sinusoidal current of peak value of 5A. (2)
- (iii) A sinusoidal ac voltage source having $v = V_m \sin(\omega t)$ is connected across an ideal capacitance C. (a) Derive an expression for X_C in terms of frequency. (b) Draw the phase relationship between current and voltage with reference to current. (c) Give the real power consumed by the circuit. (3+1+1)

Q3. [CO2]

- (i) What do you understand by time constant (τ) in inductive circuit? How does it affect the rise and decay of current in an RL circuit? Draw the IV/VI relationship curves. (2+1+1)
- (ii) At $t=0$, suddenly a dc supply of 20 V is applied to a series RL circuit having $R=11 \Omega$ and $L = 20$ H. Determine (a) the time constant of the circuit (b) initial rate of change of current (c) current at $t=2.5s$. (1+1+2)