

Dr. Shrivati

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -2 EXAMINATION- October 2019

B.Tech III Semester (ECE)

COURSE CODE: 18B11EC312

MAX. MARKS: 25

COURSE NAME: DIGITAL ELECTRONICS AND LOGIC DESIGN

COURSE CREDITS: 04

MAX. TIME: 1Hr 30 min

Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.

- For given function  $f(A, B, C, D) = \sum m(2, 3, 4, 5, 7, 8, 10, 13, 15)$  find the following.
  - Realize the minimized expression using NOR gate
  - Implement the function using 4:16 decoder [2.5 + 2.5 = 5] [CO3]
- Use Karnaugh maps to find the minimum-cost SOP and POS expressions for the function  $f(x_1, x_2, x_3, x_4) = \overline{x_1 x_3 x_4} + x_3 x_4 + \overline{x_1 x_2 x_4} + x_1 x_2 \overline{x_3 x_4}$  assuming that there are also don't-cares defined as  $d = (8, 9, 12, 13)$ . [2.5 + 2.5 = 5] [CO3]
- In a certain application, four inputs A, B, C, D (both true and complement forms available) are fed to logic circuit producing an output F, which operates a relay. The relay turns ON when  $f(A, B, C, D) = 1$  for the following states of inputs (ABCD): 0000, 0010, 0101, 0110, 1101, and 1110. States 1000 and 1001 do not occur and for the remaining states the relay is OFF. Implement the logic function using 4:1 multiplexer. [5] [CO3, CO4]
- Design a parity generator to generate even parity bit for a 3 bit word using 1:8 demultiplexer. Which other combinational circuit gives the same output.
  - Design a combinational circuit to perform the operation:  $587 - 425$ .
  - Implement 4 bit prime number detector using AOI logic. [2 + 1.5 + 1.5 = 5] [CO4]
- Give the Boolean expression of F shown in fig 1 implemented by the given CMOS logic
  - Assuming each transistor as an ideal switch, specify the states (ON state or OFF State) of each transistor when  $A = C = \text{Logic 1}$ , while  $B = D = \text{Logic 0}$ .
  - Explain the four regions in which BJT works by specifying input and output.
  - Draw a diagram of Diode Transistor Logic.

[1 + 1 + 1 + 2 = 5] [CO1, CO2]

Fig 1

