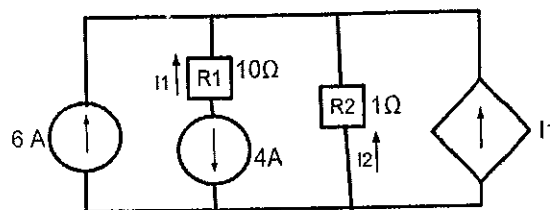


Note: All questions are compulsory. Marks are indicated against each question in square brackets.

Q1. Explain the current division rule with the help of a suitable circuit diagram.

[3]

Q2. Using Nodal Analysis, determine the value of I_2 in the circuit given below:



[3]

Q3. State Superposition theorem and explain it with the help of a suitable circuit diagram.


[3]

Q4. Prove that energy stored in the inductor is –

$$w_L(t) = \frac{1}{2} Li^2$$


[2]

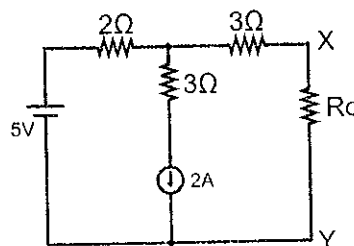Q5 Considering R_o as load resistance, determine the Norton Resistance and Norton Current across terminals X-Y terminals:




[2+3=5]

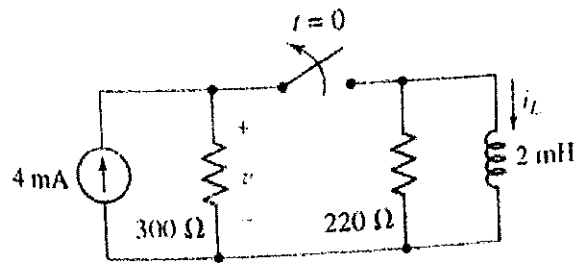Q6. With the assumption that the switch in the circuit given below has been closed a long, long, long time, calculate $i_L(t)$ at (a) the instant just before the switch opens; (b) $t=78.8 \mu\text{s}$.




[3]

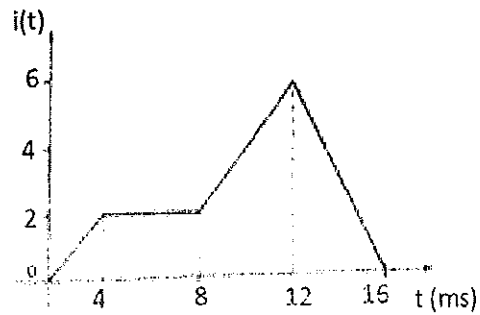Q7 The current across the inductor of 5mH is shown in the figure given below. Draw the waveform for the voltage across the inductor.



[3]

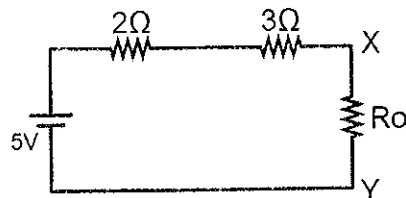Q8. Determine the value of R_o to deliver Maximum power to the resistor, R_o :



[3]