

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST-3 EXAMINATION- MAY-2023

B.Tech-VIII Semester (ECE)

COURSE CODE (CREDITS): 19B1WEC832 (3)

MAX. MARKS: 35

COURSE NAME: CAD Algorithms for Synthesis of Digital Systems

COURSE INSTRUCTOR: Dr. Pardeep Garg

MAX. TIME: 2 hours

*Note: All questions are compulsory. Marks are indicated against each question in square brackets. CO indicates Course Outcomes.*

**Q1(i).** Obtain binary decision diagram (BDD) for the function (F) by following the variable expansion sequence as  $a > b > c$ :

$$F(a, b, c) = a \cdot b + \bar{a} \cdot c + a \cdot \bar{b} \cdot c \quad [\text{CO-4, 2.5 marks}]$$

**Q1(ii).** Does the variable ordering for expansion in BDD affect the size of BDD? Discuss with the help of a suitable example. [CO-4, 1.5 marks]

**Q1(iii).** What are the basic rules which are followed in reducing the size of BDD to obtain ROBDD. Obtain the ROBDD structure of the result obtained in Q1(i). [CO-4, 3 marks]


**Q1(iv).** One of the applications of BDDs is in the synthesis of systems. In this context, show the realization of result obtained in Q1(iii) part using 2:1 multiplexers. [CO-4, 2 marks]

**Q2(i).** Why is decomposition of any given function done? Discuss the functioning of Ashenhurst, Curtis, and non-disjoint decomposition with a suitable example for each of these.

[CO-4, 0.5+1+1+1=3.5 marks]

**Q2(ii).** Compute the Boolean decomposition using Ashenhurst, Curtis decomposition for the following function:  $F(a, b, c, d) = a \cdot \bar{b} \cdot \bar{c} \cdot \bar{d} + a \cdot \bar{b} \cdot c \cdot d + \bar{a} \cdot b \cdot \bar{c} \cdot \bar{d} + \bar{a} \cdot b \cdot c \cdot d + a \cdot b \cdot \bar{c} + \bar{a} \cdot \bar{b} \cdot \bar{c}$  [CO-4, 3.5 marks]

**Q3.** Discuss the term Fusion in the context of graph theory. Obtain the fused graph corresponding to vertices a, and b in the **Figure 1**: [CO-2, 1+1=2 marks]

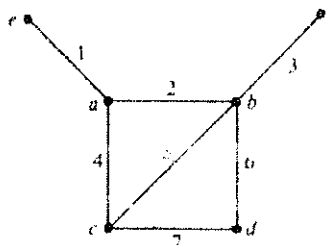

**Figure 1**

Q4. Compute the minimal expression using Quine-McCluskey method for the following expression:

$$f = \sum m(1, 2, 3, 5, 6, 7, 8, 9, 12, 13, 15) \quad [\text{CO-2, 5.5 marks}]$$

Q5. Discuss the concept of false path in VLSI employing suitable examples of multiplexer and flip-flop. [CO-5, 3 marks]

Q6. Discuss the concept of retiming w.r.t. delay in digital systems. [CO-5, 3 marks]

Q7. Why minimization of sequential circuits is required? Obtain the state table, reduced state table, reduced state diagram for the state machine whose state diagram is shown in Figure 2.

[CO-3, 1+1.5+1.5+1.5=3.5 marks]

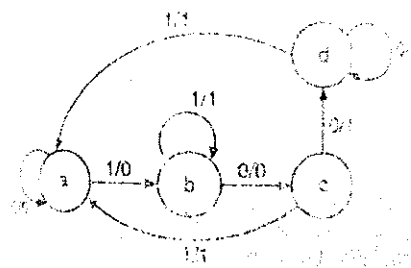


Figure 2