

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -3 EXAMINATION- 2023

B.Tech- VI Semester (ECE)

COURSE CODE (CREDITS): 18B11EC612 (3)

MAX. MARKS: 35

COURSE NAME: VLSI Technology

COURSE INSTRUCTORS: Dr. Harsh Sohal

MAX. TIME: 2 Hours

Note: (a) All questions are compulsory.

(b) Marks are indicated against each question in square brackets.

(c) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems

Q1. [CO1+CO2][7]

(a) Why the input resistance of a CMOS inverter is infinite? [1]


(b) List the differences between BJT and MOSFET. [2]

(c) Explain the formation of Inversion layer in an n channel MOSFET (use diagrams). [2]


(d) You are given a wafer of the size of 30 cm, die size of 2.5 cm<sup>2</sup>, with 1 defects/cm<sup>2</sup>;  $\alpha$  (the measure of manufacturing process complexity)=3. Cost of the wafer is INR 100,000. Calculate: (i) dies per wafer (ii) die yield [1+1]

 Q2. [CO2+CO3] [7]

For the inverter circuits given below derive the expression for  $V_{OH}$  for both (a) and (b). Which of the two shall give better output voltage swing? Explain. [3]



(a)

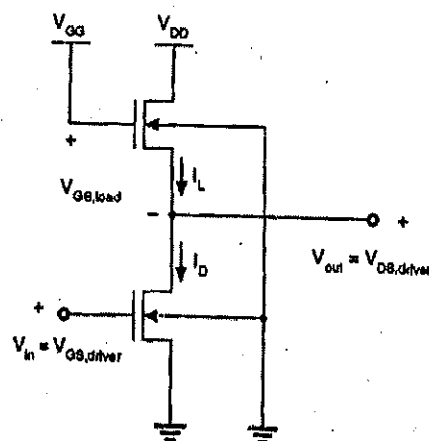

(b)

(b) [2+2]

For the circuit in Figure (b) above list the region of the operation of the load transistor and the driver transistor for the following values of I/P and O/P voltages.

V <sub>in</sub>	V <sub>out</sub>	Driver Operating Region	Load Operating region
V <sub>OL</sub>	V <sub>OH</sub>	?	?
V <sub>IL</sub>	≈ V <sub>OH</sub>	?	?
V <sub>IH</sub>	Small (slightly greater than V <sub>OL</sub> )	?	?
V <sub>OH</sub>	V <sub>OL</sub>	?	?

Q3. [CO3+CO4][8]

(a) Given  $V_{DD} = 2.5 \text{ V}$ ,  $k' = 40 \mu\text{A/V}^2$ , and  $V_{T0} = 0.5 \text{ V}$ , design a resistive-load inverter circuit with  $V_{OL} = 0.1 \text{ V}$ .

(i) Determine the (W/L) ratio of the driver transistor and the value of the load resistor  $R_L$  that achieves the required  $V_{OL}$ . [3]

Calculate the DC power dissipation of the inverter above (assuming that the input voltage is "low" during 50% of the operation time, and "high" during the remaining 50%) when  $W/L = 1$ . [1]

(b) Consider a CMOS inverter circuit with the following parameters: [2+2]

$$V_{DD} = 5 \text{ V}$$

$$V_{T0,n} = 1 \text{ V}$$

$$V_{T0,p} = -1 \text{ V}$$


$$k_n = 200 \mu\text{A/V}^2$$

$$k_p = 80 \mu\text{A/V}^2$$


Calculate (i) Noise Margin Low (NML) (ii) Threshold voltage ( $V_{TH}$ ) of the CMOS inverter

Q4. [CO5, CO6][6]

 
(a) Calculate the minimum supply voltage ( $V_{DD}$  in Volts) required for the transistor M1 to operate in saturation mode. Consider the following quantities given for the nMOS:  $K_n = \mu_n C_{ox} (W/L) = 1 \text{ mA/V}^2$ ;  $V_{THN} = 1.9 \text{ V}$  both the transistors. Assume that the channel length modulation is zero and the body is shorted to the source. [2]



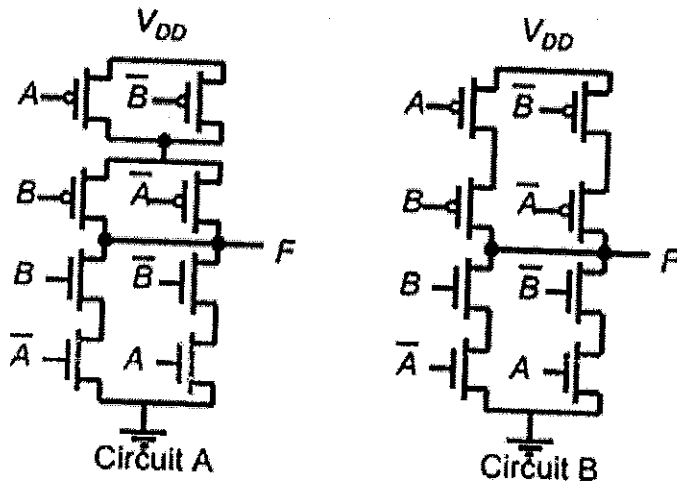(b) Write the Boolean equations being implemented by the circuits given below. (1+1)



 (c) What is the logic being implemented by the circuit below? What is the logic style used? List its comparison with static CMOS logic implementation. [2]



Q5. [CO5, CO6] [7]

(a) Implement the Boolean function  $F = \overline{(D + E + A)(B + C)}$  using static CMOS logic and draw the corresponding circuit diagram. [2]

- (b) Find an equivalent CMOS inverter circuit for the above implementation in (a) for simultaneous switching of all inputs, assuming that  $(W/L)_p = 15$  for all pMOS transistors and  $(W/L)_n = 10$  for all nMOS transistors. [2]
- (c) Determine the Boolean function being implemented by the following Transmission gate implementation while writing intermediate equations. [3]

